

七段数码管动态显示电路设计

Pb16060240

黄骏达

实验目的:

1. 熟悉 8 位七段数码管动态显示的控制
2. 熟练掌握 VHDL test bench 的编写和仿真流程
3. 熟练掌握 Altera FPGA 的开发环境、设计步骤和流程

8 位数码管原理:

1. 首先七段数码管由 7 位数据信号进行内容控制，七位数据总线分别控制七段数码管的一段，当数码管为共阳极数码管时，数码管的所有阳极共线，并连接在高电平上。


 



图 1 七段数码管构成图

 2. 8 位是指需要同时控制 8 个七位数码管进行输出，通过一个控制器，轮流扫描 8 个数码管，即可实现 8 个数码管的轮流显示。




实验设计：

1. 如下为模块化电路设计基本架构：

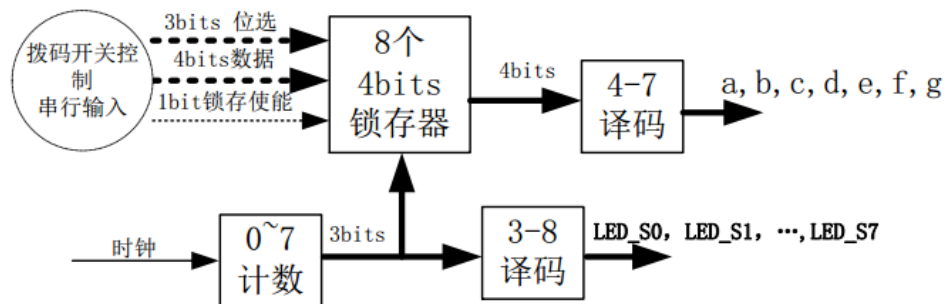


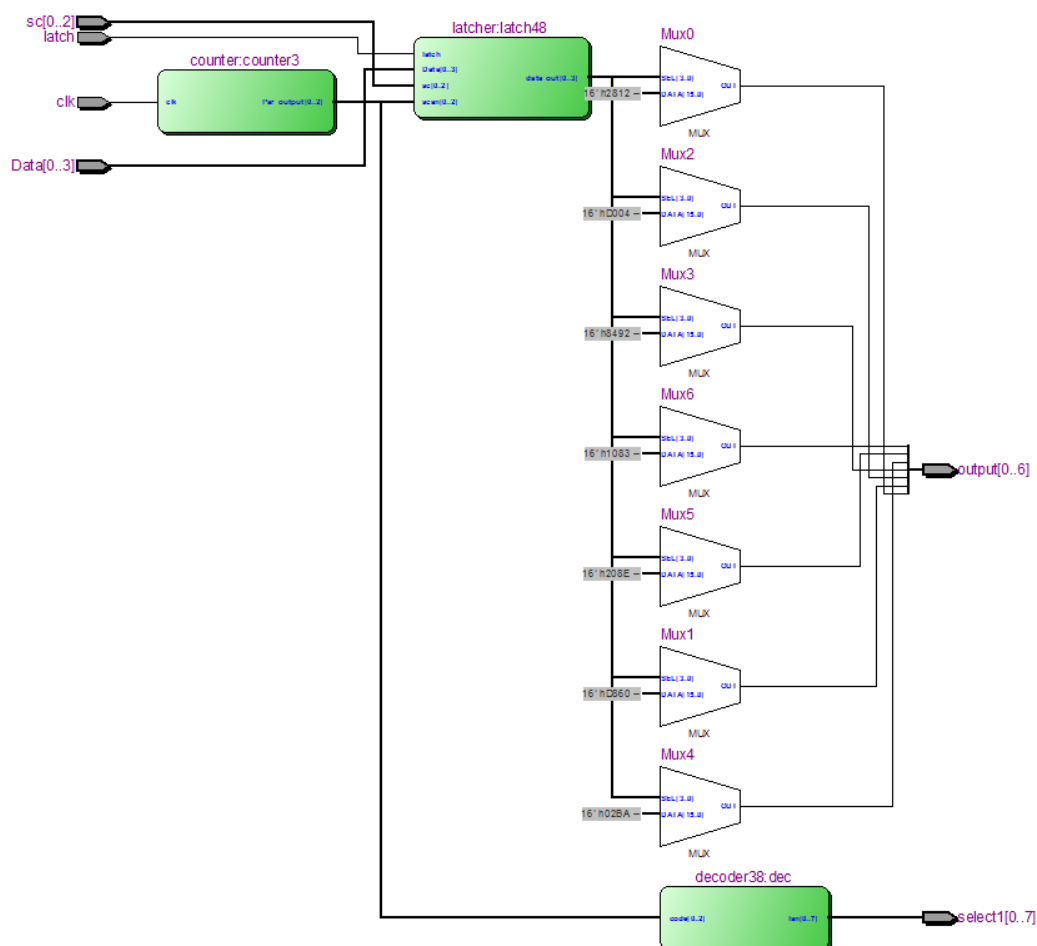2. 首先设计 4-7 译码器，并将 4-7 译码器作为顶层实体，电路图如下所示：




3. 设计锁存器，锁存器能够被 4 位输入进行控制，其中 1 位控制数据信号的锁存，其中 3 位实现对于 8 个内部虚拟锁存器的选择。然后由 4 位数据输入，将数码管上的显示数据锁存在这 8 个内部虚拟锁存器的其中之一之中。由于锁存器电路较为复杂，将在后面贴出。

 4. 另一部分是扫描电路，扫描电路由一个分频器，一个 8 进制计数器和一个 3-8 译码器组成。
5. 分频器将初始 50m 时钟进行分频输出，电路如下所示（不过，分频器在此可有可无）：



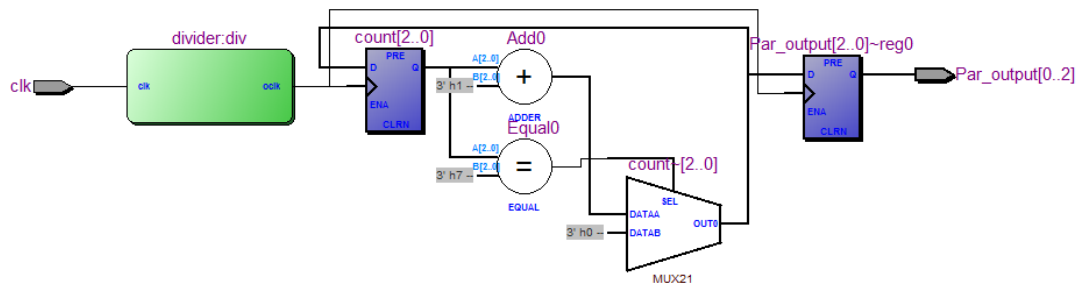
6. 8 进制计数器将分频器的分频时钟输出进行计数, 并将数值一个输出给锁存器, 进行数码管映射数据的扫描信号, 一个输出给 3-8 译码器, 八进制计数器电路图如下所示:



7. 3-8 译码器负责将 3 位八进制计数器的输出进行译码并输出给数码管选择控制总线，在此次电路设计中，由于已经完全掌握使用 `case` 来进行译码，因此使用了 `others` 与 `for` 循环进行组合，降低了编写代码的复杂度，但同时在电路中发现，尽管代码简洁，但电路相对于 `case` 的电路复杂很多，因此并不推崇使用，电路附后。


电路图：

- 锁存器

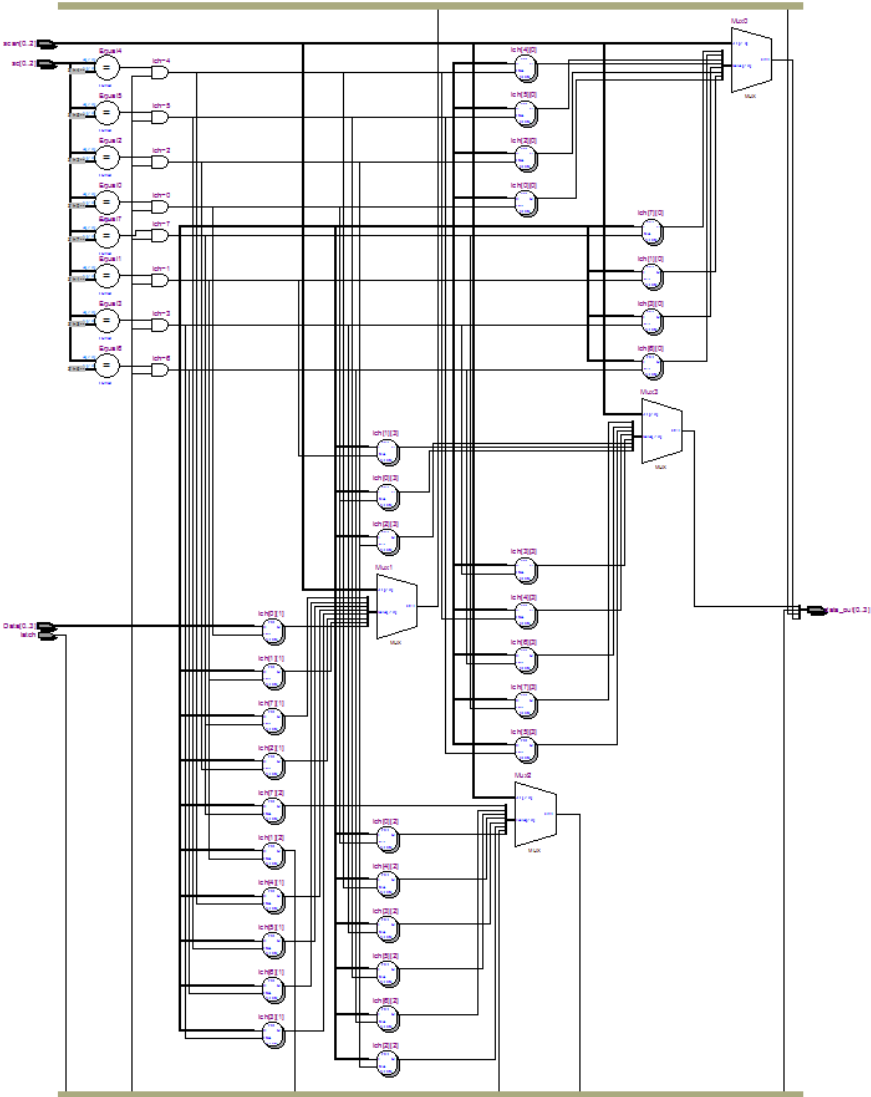

● 38 译码器

(由于使用新方法，因此电路复杂，并不推崇)

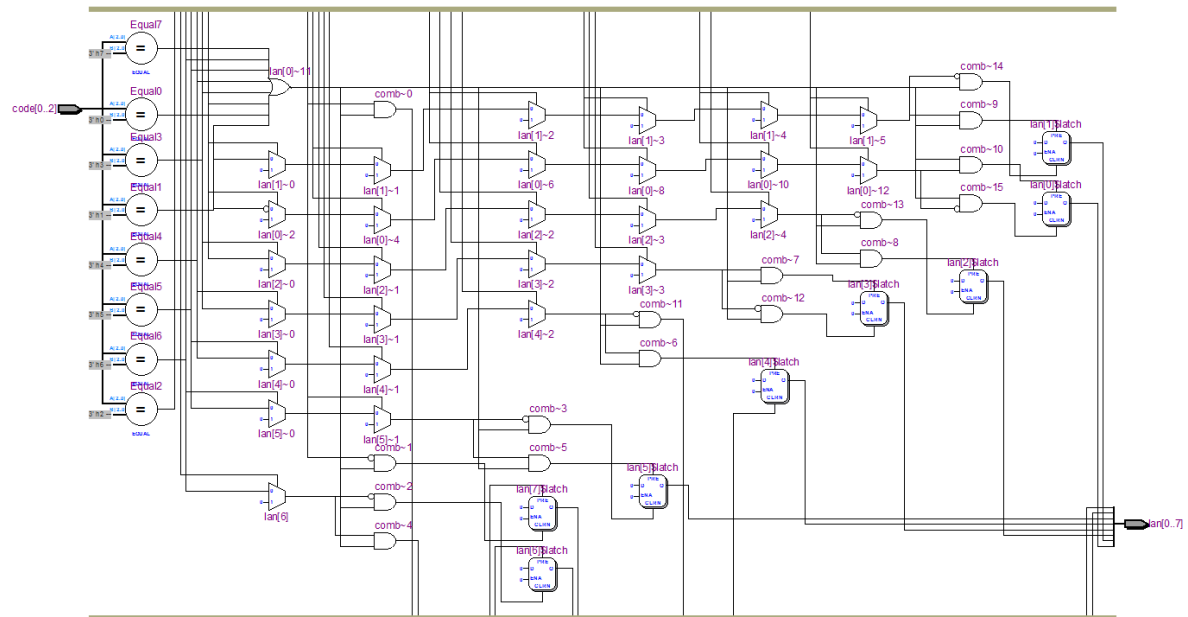

VHDL 源代码:

(counter.vhd)8 进制计数器

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
use ieee.std_logic_arith.all;
```

```
entity counter is
```

```
port(clk : in std_logic;
```

```
      Par_output : out std_logic_vector(0 to 2));
```

```
end entity;
```

```
architecture behave of counter is
```

```
    component divider is
```

```
        port (clk : IN std_logic;
```

```
              oclk : OUT std_logic);
```

```
    end component;
```

```
    signal fclk : std_logic;
```

```
begin
```

```
    div : divider port map (clk,fclk);
```

```
    process(fclk)
```

```

variable count : integer range 0 to 7 := 0;
begin
    if (fclk'event and fclk = '1') then
        if (count = 7 ) then
            count := 0;
        else
            count := count + 1;
        end if;
        Par_output <= conv_std_logic_vector(count,3);
    end if;
end process;
end behave;

```

(decoder38.vhd)3-8 译码器

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity decoder38 is
port(code : in std_logic_vector(0 to 2);
      lan : out std_logic_vector(0 to 7));
end entity decoder38;

```

architecture behave of decoder38 is

```

begin
    process(code)
    begin

        for i in 0 to 7 loop
            if (code = conv_std_logic_vector(i,3)) then
                lan <= ( i => '1',others => '0');
            end if;
        end loop;

    end process;
end behave;

```

(Digital.vhd)顶层实体： 4-7 译码器

```

library ieee;
use ieee.std_logic_1164.all;

entity digital is --47
port(Data : in std_logic_vector(0 to 3);

```

```

        sc : in std_logic_vector(0 to 2);
        latch : in std_logic;
        output: out std_logic_vector(0 to 6);
        clk : in std_logic;
        select1 : out std_logic_vector(0 to 7));

end entity;

architecture behave of digital is

component counter is
port(clk : in std_logic;
      Par_output : out std_logic_vector(0 to 2));
end component;

component latcher is
port(Data : in std_logic_vector(0 to 3);
      sc : in std_logic_vector(0 to 2);
      latch : in std_logic;
      scan : in std_logic_vector(0 to 2);
      data_out: out std_logic_vector(0 to 3));
end component;

component decoder38 is
port(code : in std_logic_vector(0 to 2);
      lan : out std_logic_vector(0 to 7));
end component;

signal data_output : std_logic_vector(0 to 3);
signal temp_bus : std_logic_vector(0 to 2);

begin

    counter3: counter port map(clk,temp_bus);
    latch48 : latcher port map (Data,sc,latch,temp_bus,data_output);
    dec : decoder38 port map(temp_bus,select1);

    process(data_output)
        variable a0:std_logic_vector(0 to 6) := "0000001";
        variable a1:std_logic_vector(0 to 6) := "1001111";
        variable a2:std_logic_vector(0 to 6) := "0010010";
        variable a3:std_logic_vector(0 to 6) := "0000110";
        variable a4:std_logic_vector(0 to 6) := "1001100";
        variable a5:std_logic_vector(0 to 6) := "0100100";
        variable a6:std_logic_vector(0 to 6) := "0100000";
    end process;

```

```

variable a7:std_logic_vector(0 to 6) := "0001111";
variable a8:std_logic_vector(0 to 6) := "0000000";
variable a9:std_logic_vector(0 to 6) := "0000100";
variable aA:std_logic_vector(0 to 6) := "0001000";
variable aB:std_logic_vector(0 to 6) := "1100000";
variable aC:std_logic_vector(0 to 6) := "0110001";
variable aD:std_logic_vector(0 to 6) := "1000010";
variable aE:std_logic_vector(0 to 6) := "0110000";
variable aF:std_logic_vector(0 to 6) := "0111000";

begin
case data_output is
    when "0000" => output <= a0;
    when "0001" => output <= a1;
    when "0010" => output <= a2;
    when "0011" => output <= a3;
    when "0100" => output <= a4;
    when "0101" => output <= a5;
    when "0110" => output <= a6;
    when "0111" => output <= a7;
    when "1000" => output <= a8;
    when "1001" => output <= a9;
    when "1010" => output <= aA;
    when "1011" => output <= aB;
    when "1100" => output <= aC;
    when "1101" => output <= aD;
    when "1110" => output <= aE;
    when "1111" => output <= aF;
    when others => output <= "XXXXXXX";
end case;
end process;
end behave;

```

(divider.vhd)分频器

```

library ieee;
use ieee.std_logic_1164.all;

entity divider is
    port (clk : IN std_logic;
          oclk : OUT std_logic);
end entity;

architecture behave of divider is
begin

```



```

process(clk)
    variable num: integer range 0 to 31;
    variable temp:std_logic := '1';
    begin
    if (clk = '1' and clk'event) then
        if (num = 10) then
            num := 0; temp := not temp; oclk <= temp;
        else num := num + 1;
        end if;
    end if;

    end process;
end behave;

```

(latcher.vhd)锁存器

```

library ieee;
use ieee.std_logic_1164.all;

entity latcher is
    port(Data : in std_logic_vector(0 to 3);
          sc : in std_logic_vector(0 to 2);
          latch : in std_logic;
          scan : in std_logic_vector(0 to 2);
          data_out: out std_logic_vector(0 to 3));
end entity latcher;

architecture behave of latcher is

    type lch_array is array(0 to 7) of std_logic_vector(0 to 3);
    signal lch : lch_array;
    signal temp: std_logic := '1';

    begin

        lch(0) <= Data when (latch = '1' and sc = "000");
        lch(1) <= Data when (latch = '1' and sc = "001");
        lch(2) <= Data when (latch = '1' and sc = "010");
        lch(3) <= Data when (latch = '1' and sc = "011");
        lch(4) <= Data when (latch = '1' and sc = "100");
        lch(5) <= Data when (latch = '1' and sc = "101");
        lch(6) <= Data when (latch = '1' and sc = "110");
        lch(7) <= Data when (latch = '1' and sc = "111");
    end

```

```

process(scan)
begin
    case scan is
        when "000" => data_out <= lch(0);
        when "001" => data_out <= lch(1);
        when "010" => data_out <= lch(2);
        when "011" => data_out <= lch(3);
        when "100" => data_out <= lch(4);
        when "101" => data_out <= lch(5);
        when "110" => data_out <= lch(6);
        when "111" => data_out <= lch(7);
        when others => data_out <= "XXXX";
    end case;
end process;

end behave;

```

(digital_tb.vhd)test bench

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity digital_tb is
end entity;

architecture bh of digital_tb is

    component Digital is
    port(Data : in std_logic_vector(0 to 3);
          sc : in std_logic_vector(0 to 2);
          latch : in std_logic;
          output: out std_logic_vector(0 to 6);
          clk : in std_logic);
    end component;

    signal data : std_logic_vector(0 to 3);
    signal sc : std_logic_vector(0 to 2);
    signal latch : std_logic;
    signal output : std_logic_vector(0 to 6);
    signal clk : std_logic;

begin

```

u1 : Digital port map (data,sc,latch,output,clk);

process

begin

clk <= '1';

wait for 10 ns;

clk <= '0';

wait for 10 ns;

end process;

process

begin

latch <= '1';

for i in 0 to 15 loop

data <= CONV_STD_LOGIC_VECTOR(i,4);

for j in 0 to 7 loop

sc <= conv_STD_LOGIC_VECTOR(j,3);

wait for 10 ns;

end loop;


wait for 10 ns;

end loop;

end process;

end bh;

仿真结果记录:

 

FPGA 验证结果记录:

Latch 所映射的开关打开到 1 时，将数据信息以及锁存器片选信息锁存进入锁存器，从而在扫描时将在对应的片选数码管上对数据进行更新。

实验总结：

1. 此次实验引入使用 arith 库，主要函数为 conv_std_logic_vector，将 integer 类型转化为 std_logic_vector 类型，从而使得很多地方能够使用 for 循环时的代码大为简化，使代码复杂度降低，但也由于未对比电路复杂度的变化，因此主要使用实在 test bench 中，从而减小对于实体电路的影响。
2. 此次实验引入 ppt 中未提及的 others 用法，out <= (l=>'1', others=>'0')，类似于位操作，将向量的 i 号位赋值 1，同时将其他位赋值 0。这种方法虽然能够避免使用 case 一类的语句从而简化代码量，但是实际上却是使得代码可读性降低，同时使电路情况变得极其复杂。
因此，从这种情况看来，这种写法最方便的是快速开发，在实际应用时非常不推崇此种代码写法。
3. 已较熟练的掌握 modelsim 来进行 debug，收获颇多，并且编写代码时间大大降低。