

# 矩阵键盘扫描设计

PB16060240


黄骏达

## 实验目的

1. 进一步学习并掌握 Quartus 设计的方法及步骤
2. 熟悉 VHDL 语言电路设计方法
3. 熟悉 VHDL test bench 的设计
4. 学习并掌握利用 VHDL 描述并设计电路的方法及步骤
5. 学习并掌握键盘阵列的扫描输入的方法及实现过程

## 键盘扫描原理：

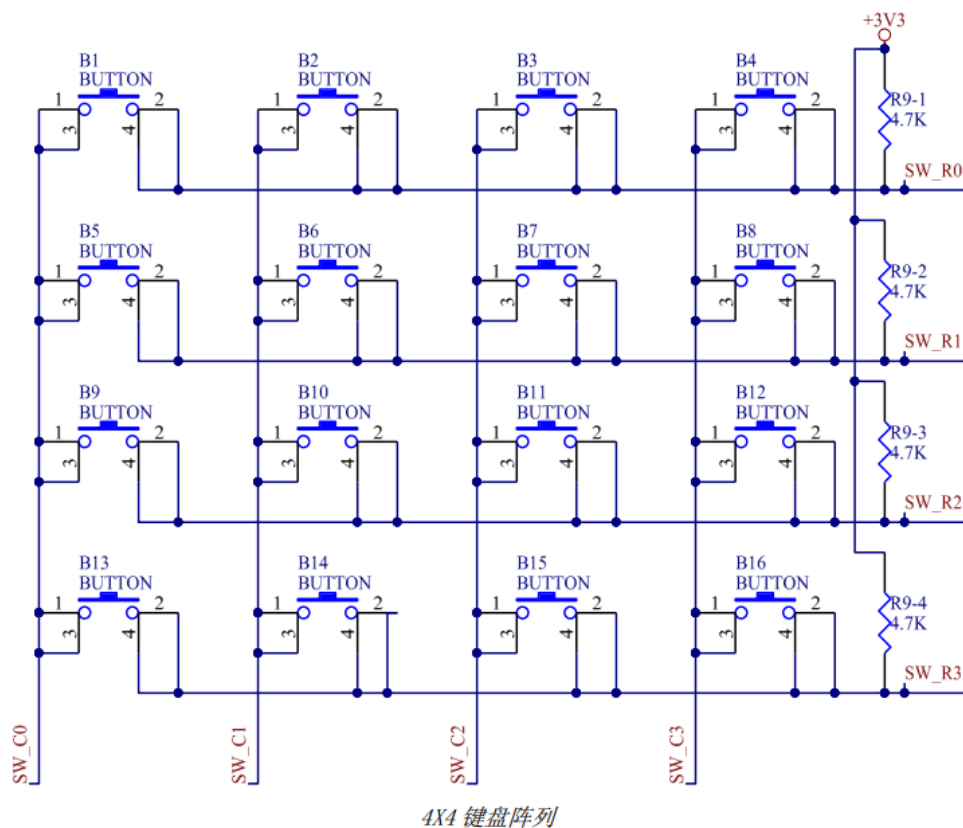1. 此次矩阵键盘是一个由 4X4 个按键开关组成的阵列，可实现 16 中状态输入，矩阵键盘阵列如下：




2. 在行输入端，由上拉电阻接到 3.3v 标准 TTL 电平上，在列输入端，列电平输出直接由控制器进行控制。


- 当按下按键，如 B1，此时，若列输出为 0111，则在行输入端能够检测到输入为 0111，这是因为，对于按键按下的行，由于电路接通，使得此行输入电平变为 0 电平，而对于没有按键按下的行，由于电路断开，因此行电平依旧被外部电压拉高在高电平状态；同时，若列输出为 1011，因为在第二列并无按键按下，因此行输入全部为高电平，即在输入端能够检测到 1111，其他列输出同理。

## 实验设计：


- 模块化电路逻辑简图如下：

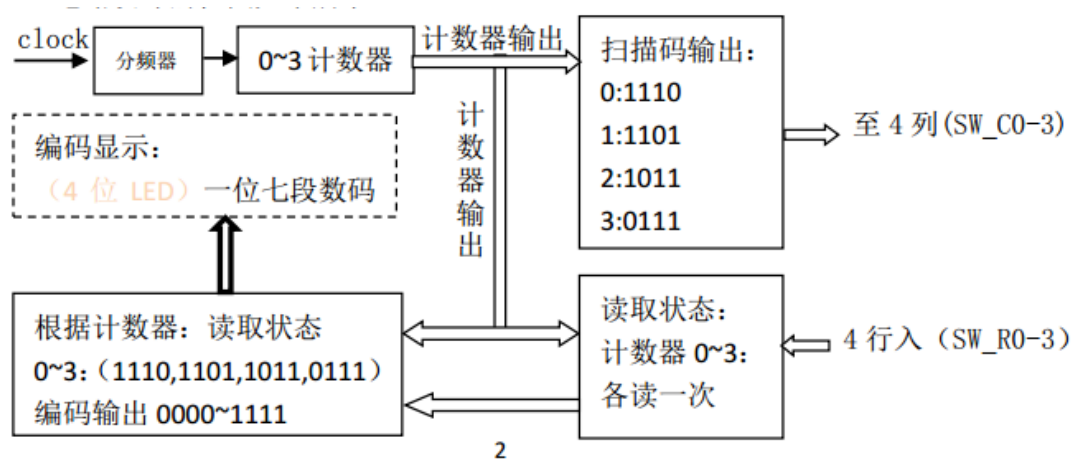

 
- 由于时钟 50MHz 太快，因此需要一个分频器进行分频，分频器电路图如下，为 200 分频：



 
- 分频器的分频信号输出至计数器，计数器再将输出输出给译码器、扫描器和读取设备，作为信号触发源，总电路图如下所示：



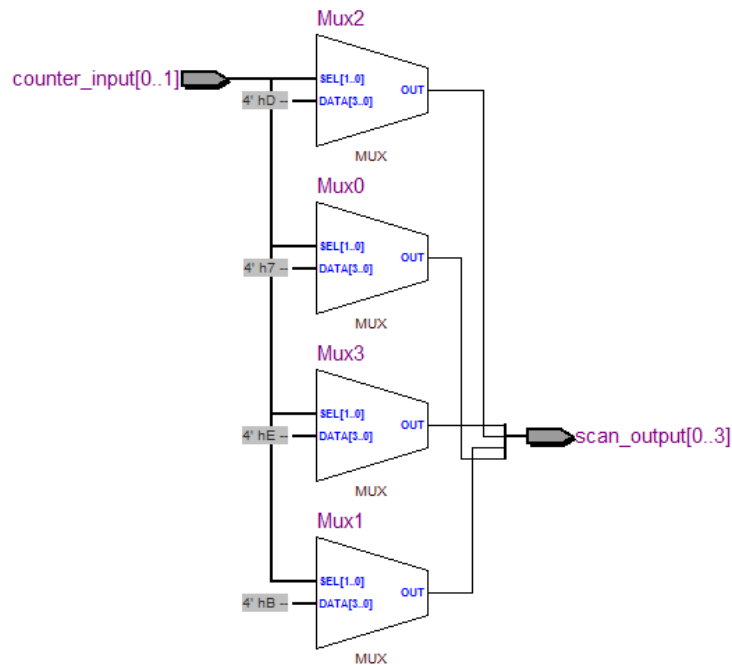- 每个计数器输出到来时，扫描器输出对应的电平，如模块逻辑图所示。同时读取设备读入行电平信号，扫描器的电路图如下所示：



 
- 然后读取设备将从键盘获取的行信息输出给译码器，译码器根据计数器的扫描信号和行信号进行译码,行输入电路图如下所示：




- 译码器译码后将显示信息输出给数码管，同时若为读取到有效的信号，则另数码管为熄灭，译码器与数码管显示电路图在后面贴出。

电路图：

译码器电路图：

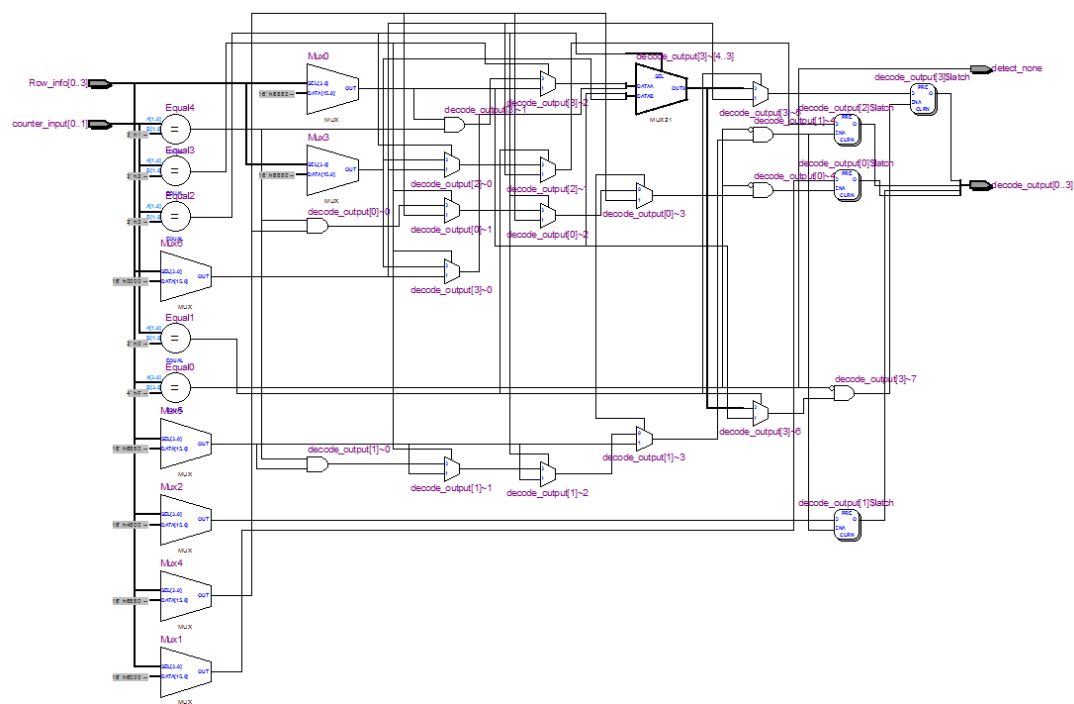

数码管控制电路：

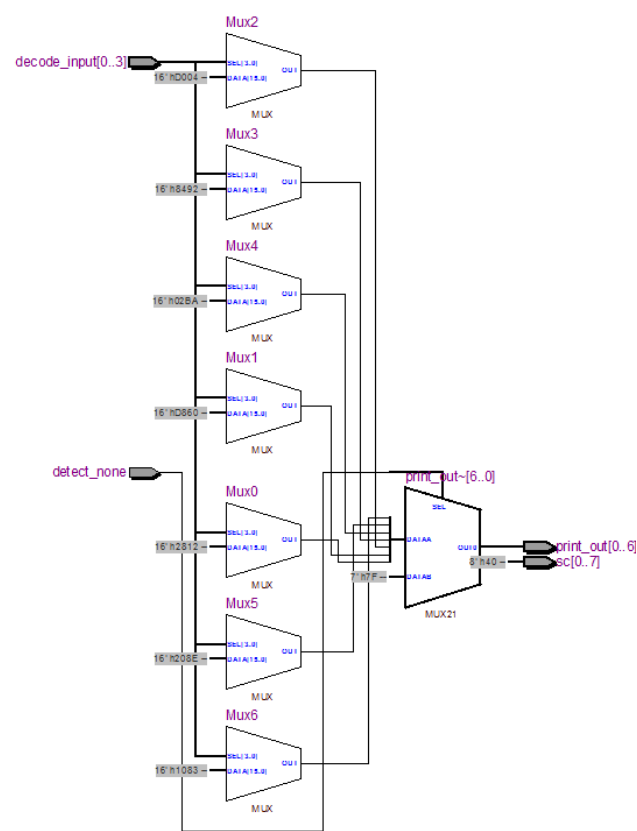

## VHDL 源代码:

### (scanner.vhd) 列扫描

```
library ieee;
use ieee.std_logic_1164.all;

entity scanner is
port(counter_input : in std_logic_vector(0 to 1);
      scan_output : out std_logic_vector(0 to 3));
end entity scanner;

architecture behave of scanner is
begin
    process(counter_input)
    begin
        case counter_input is
            when "00" => scan_output <= "1110";
            when "01" => scan_output <= "1101";
            when "10" => scan_output <= "1011";
            when "11" => scan_output <= "0111";
            when others => NULL;
        end case;
    end process;
end behave;
```

### (reader.vhd) 行读入

```
library ieee;
use ieee.std_logic_1164.all;

entity reader is
port(fclk : in std_logic;
      Row_input : in std_logic_vector(0 to 3);
      Row_info : out std_logic_vector(0 to 3));
end entity reader;

architecture behave of reader is
begin
    process(fclk)
    begin
        if rising_edge(fclk) then
            Row_info <= Row_input;
        end if;
    end process;
end behave;
```

### **(print.vhd) 数码管控制**

```
library ieee;
use ieee.std_logic_1164.all;

entity print is
port(decode_input : in std_logic_vector(0 to 3);
      sc : out std_logic_vector(0 to 7);
      print_out : out std_logic_vector(0 to 6);
      detect_none : in std_logic);
end entity print;

architecture behave of print is
begin
    sc <= "01000000";
    process(decode_input,detect_none)
        variable a0:std_logic_vector(0 to 6) := "0000001";
        variable a1:std_logic_vector(0 to 6) := "1001111";
        variable a2:std_logic_vector(0 to 6) := "0010010";
        variable a3:std_logic_vector(0 to 6) := "0000110";
        variable a4:std_logic_vector(0 to 6) := "1001100";
        variable a5:std_logic_vector(0 to 6) := "0100100";
        variable a6:std_logic_vector(0 to 6) := "0100000";
        variable a7:std_logic_vector(0 to 6) := "0001111";
        variable a8:std_logic_vector(0 to 6) := "0000000";
        variable a9:std_logic_vector(0 to 6) := "0000100";
        variable aA:std_logic_vector(0 to 6) := "0001000";
        variable aB:std_logic_vector(0 to 6) := "1100000";
        variable aC:std_logic_vector(0 to 6) := "0110001";
        variable aD:std_logic_vector(0 to 6) := "1000010";
        variable aE:std_logic_vector(0 to 6) := "0110000";
        variable aF:std_logic_vector(0 to 6) := "0111000";
    begin
        if(detect_none = '1') then
            print_out <= "1111111";
        else
            case decode_input is
                when "0000" => print_out <= a0;
                when "0001" => print_out <= a1;
                when "0010" => print_out <= a2;
                when "0011" => print_out <= a3;
                when "0100" => print_out <= a4;
                when "0101" => print_out <= a5;
                when "0110" => print_out <= a6;
```

```

        when "0111" => print_out <= a7;
        when "1000" => print_out <= a8;
        when "1001" => print_out <= a9;
        when "1010" => print_out <= aA;
        when "1011" => print_out <= aB;
        when "1100" => print_out <= aC;
        when "1101" => print_out <= aD;
        when "1110" => print_out <= aE;
        when "1111" => print_out <= aF;
        when others => print_out <= "1111111";
    end case;
end if;
end process;
end behave;

```

### **(decoder.vhd) 译码器**

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity decoder is
    port(counter_input : in std_logic_vector(0 to 1);
          Row_info : in std_logic_vector(0 to 3);
          decode_output: out std_logic_vector(0 to 3);
          detect_none : out std_logic);
end entity decoder;

```

architecture behave of decoder is

begin

```

    process(counter_input,Row_info)

    begin
        if (Row_info = "1111") then
            detect_none <= '1';
        else
            detect_none <= '0';
            if (counter_input = "00") then --10
                case Row_info is
                    when "0111" => decode_output <= conv_std_logic_vector(0,4);
                    when "1011" => decode_output <= conv_std_logic_vector(4,4);
                    when "1101" => decode_output <= conv_std_logic_vector(8,4);
                    when "1110" => decode_output <= conv_std_logic_vector(12,4);

```

```

        when others => NULL;
    end case;
elsif (counter_input = "11") then --01
    case Row_info is
        when "0111" => decode_output <= conv_std_logic_vector(1,4);
        when "1011" => decode_output <= conv_std_logic_vector(5,4);
        when "1101" => decode_output <= conv_std_logic_vector(9,4);
        when "1110" => decode_output <= conv_std_logic_vector(13,4);
        when others => NULL;
    end case;
elsif (counter_input = "10") then --00
    case Row_info is
        when "0111" => decode_output <= conv_std_logic_vector(2,4);
        when "1011" => decode_output <= conv_std_logic_vector(6,4);
        when "1101" => decode_output <= conv_std_logic_vector(10,4);
        when "1110" => decode_output <= conv_std_logic_vector(14,4);
        when others => NULL;
    end case;
elsif (counter_input = "01") then --11
    case Row_info is
        when "0111" => decode_output <= conv_std_logic_vector(3,4);
        when "1011" => decode_output <= conv_std_logic_vector(7,4);
        when "1101" => decode_output <= conv_std_logic_vector(11,4);
        when "1110" => decode_output <= conv_std_logic_vector(15,4);
        when others => NULL;
    end case;
end if;
end if;
end process;

end behave;

```

### **(counter.vhd) 计数器**

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity counter is
    port(fclk : in std_logic;
         counter_output : out std_logic_vector(0 to 1));
end entity counter;

architecture behave of counter is

```



```

begin
    process(fclk)
        variable temp : std_logic_vector(0 to 1) := "00";
        begin
            if (rising_edge(fclk)) then
                temp := temp + 1;
            end if;
            counter_output <= temp;
        end process;
    end behave;

```

### **(Keyboard.vhd) 顶层实体**

```

library ieee;
use ieee.std_logic_1164.all;

entity Keyboard is
    port(clk : in std_logic;
          scanner_out : out std_logic_vector(0 to 3);
          Row_input : in std_logic_vector(0 to 3);
          Digital_sc : out std_logic_vector(0 to 7);
          Digital_output : out std_logic_vector(0 to 6));
end entity Keyboard;

architecture behave of Keyboard is

    component divider is
        port(clk : in std_logic;
              fclk : out std_logic);
    end component divider;

    component counter is
        port(fclk : in std_logic;
              counter_output : out std_logic_vector(0 to 1));
    end component counter;

    component scanner is
        port(counter_input : in std_logic_vector(0 to 1);
              scan_output : out std_logic_vector(0 to 3));
    end component scanner;

    component reader is
        port(fclk : in std_logic;
              Row_input : in std_logic_vector(0 to 3);
              Row_info : out std_logic_vector(0 to 3));
    end component reader;

```

```

end component reader;

component decoder is
port(counter_input : in std_logic_vector(0 to 1);
      Row_info : in std_logic_vector(0 to 3);
      decode_output: out std_logic_vector(0 to 3);
      detect_none : out std_logic);
end component decoder;

component print is
port(decode_input : in std_logic_vector(0 to 3);
      sc : out std_logic_vector(0 to 7);
      print_out : out std_logic_vector(0 to 6);
      detect_none : in std_logic);
end component print;

signal counter_bus : std_logic_vector(0 to 1);
signal Row_info_bus : std_logic_vector(0 to 3);
signal code_bus : std_logic_vector(0 to 3);
signal detect_none : std_logic;
signal fclk : std_logic;

begin
divider1 : divider port map(clk, fclk);
counter1 : counter port map(fclk , counter_bus);
scanner1 : scanner port map(counter_bus, scanner_out);
reader1 : reader port map(fclk, Row_input, Row_info_bus);
decoder1 : decoder port map(counter_bus, Row_info_bus, code_bus, detect_none);
print1 : print port map(code_bus, Digital_sc, Digital_output, detect_none);

end behave;

```

### **(Keyboard\_tb.vhd) 测试板**

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity Keyboard_tb is
end entity;

architecture behavior of Keyboard_tb is

```

```

component Keyboard is
port(clk : in std_logic;
      scanner_out : out std_logic_vector(0 to 3);
      Row_input : in std_logic_vector(0 to 3);
      Digital_sc : out std_logic_vector(0 to 7);
      Digital_output : out std_logic_vector(0 to 6));
end component;

signal clk : std_logic;
signal scan : std_logic_vector(0 to 3);
signal row_input : std_logic_vector(0 to 3);
signal digital_sc : std_logic_vector(0 to 7);
signal digital_output : std_logic_vector(0 to 6);

begin
main : Keyboard port map(clk, scan, row_input,digital_sc, digital_output);

    process
    begin
        clk <= '1';
        wait for 10 ns;
        clk <= '0';
        wait for 10 ns;
    end process;

    process
    begin
        for j in 0 to 3 loop
            row_input <= (j => '0' , others => '1');
            wait for 20 ns;
            for i in 0 to 3 loop
                if (i /= j) then
                    row_input <= (others => '1');
                    wait for 20 ns;
                end if;
            end loop;
        end loop;
    end process;

end behavior;

```

### **(divider.vhd) 分频器**

```

library ieee;
use ieee.std_logic_1164.all;


```

```

entity divider is
port(clk : in std_logic;
      fclk : out std_logic);
end entity divider;
architecture behave of divider is
begin
    process(clk)
        variable temp : integer range 0 to 100 := 0;
        variable sign : std_logic := '0';
    begin
        if (rising_edge(clk)) then
            temp := temp + 1;
            if(temp = 100) then
                temp := 0;
                fclk <= sign;
                sign := not sign;
            end if;
        end if;
    end process;
end behave;

```

## 仿真结果记录:

 

## FPGA 验证结果:

按下按键，在数码管上显示对应按键的编码，若未按下按键，按键不显示。

## 实验总结:

1. 前几次测试没有加分频器，直接将 50MHz 时钟信号引入计数器。但是这样会出现问题，具体原因还不是很清楚，表现是，数码管显示 0，并且按下按键，部分按键按下后数码管的显示会有轻微变化，但是主要还是显示 0。加上分频器之后问题自动解决。
2. 程序写入时出现 fail，主要是 USB 端口的连线问题导致。